

**In The Name Of God**

**University of Tehran**

Department of Engineering Science

Algorithms of Machine Learning

Spring 2022

## **Project 3**


**Professor: Dr. Ali Kamandi**

Students: Abbas Mohamadiyan 810898059

Mohamad Esfandiyarpoor 8108980

1. Well, as you can see, the codes and diagrams are corresponding.

## OAI1

 

```
timescale 1ns/1ns


module OAI1 (input a,b,c, output w);

    wire x,y;
    supply1 Vdd;
    supply0 Gnd;

    pmos #(5,6,7) T1(w, Vdd, c);
    pmos #(5,6,7) T2(x, Vdd, a);
    pmos #(5,6,7) T3(w, x, b);
    nmos #(3,4,5) T4(y, Gnd, b);
    nmos #(3,4,5) T5(y, Gnd, a);
    nmos #(3,4,5) T6(w, y, c);

endmodule
```

## Nor

 

```
timescale 1ns/1ns

module Nor (input a,b , output w);


    wire x;

    supply1 Vdd;
    supply0 Gnd;

    pmos #(5,6,7) T1(x, Vdd, a);
    pmos #(5,6,7) T2(w, x, b);
    nmos #(3,4,5) T3(w, Gnd, b);
    nmos #(3,4,5) T4(w, Gnd, a);


endmodule
```

inverter

 

 2.


```
timescale 1ns/1ns
module Inv (input a, output w);
    supply1 Vdd;
    supply0 Gnd;
    pmos #(5,6,7) T1(w, Vdd, a);
    nmos #(3,4,5) T2(w, Gnd, a);
endmodule
```



```
timescale 1ns/1ns
module OAI2 (input a,b,c, output w);
    wire x,y,z;
    Inv I1(.a(c), .w(y));
    Nor N1(.a(a), .b(b), .w(x));
    Nor N2(.a(x), .b(y), .w(z));
    Inv I2(.a(z), .w(w));
endmodule
```

3. for OAI1 I believe the worse case delay happens when T2 and T3 transistors change(to 1) and it happens when T3 conducts(b=0) but T2 changes and c = 1 and it's 10 Ns (5+5 to1) and this in the case of OAI2 is 29 Ns ! which is a lot worse! according to the wave form but my calculation says it should be 25 (2\*10 Ns for Nors and 5 Ns for inversion) for to0 case it holding the previous situation we change b to 1 for OAI1 it would be 8NS and for OAI2 it's 24(according to the

critical path)

 

```
timescale 1ns/1ns

module test12;
    reg a, b, c;
    wire w1, w2;

    OAI1 sample1(.a(a), .b(b), .c(c), .w(w1));
    OAI2 sample2(.a(a), .b(b), .c(c), .w(w2));

    initial begin
        $dumpfile("OAI12TB.vcd");
        $dumpvars(0, test12);
        c = 1;
        a = 1;
        b = 0;
        #40 a = 0;

        #40 b = 1;
        #40 $finish;
    end
endmodule
```

4. mmmmm report is incomplete but it's due to the lack of time but codes are all complete sorry